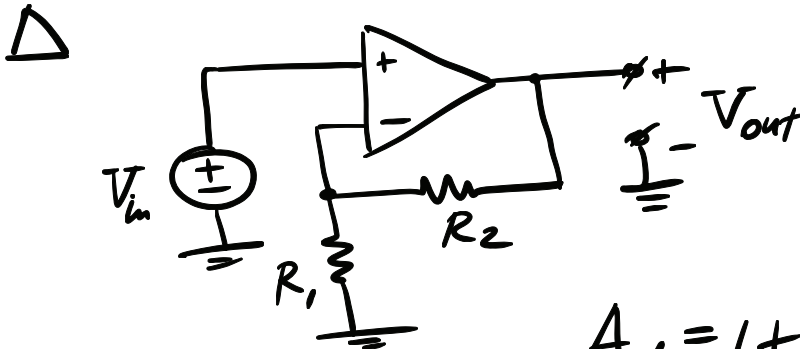


HOMEWORK 4

SOLUTIONS

Problem 1

Design a non-inverting amplifier that will boost the input voltage of $V_{in} = 200 \text{ mV}$ to $V_{out} = 3.3 \text{ V}$.




$$A_v = 1 + \frac{R_2}{R_1} = \frac{V_{out}}{V_{in}} = \frac{3.3\text{V}}{200\text{mV}} = 16.5 \frac{\text{V}}{\text{V}}$$

So that,

$$\frac{R_2}{R_1} = 15.5$$

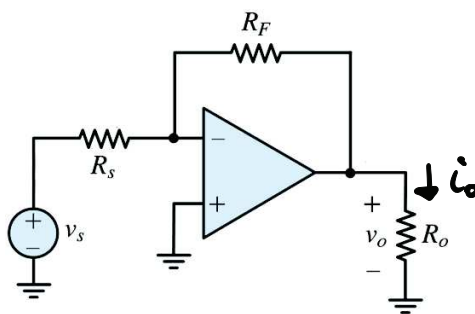Choosing $R_1 = 1\text{k} \Rightarrow R_2 = 15.5\text{k}$



Problem 2**Figure P2**


Determine the output ~~current~~^{voltage} v_o and current i_o in the circuit of **Figure P2**. Assume $R_s = 1.7 \text{ k}\Omega$, $R_F = 5.1 \text{ k}\Omega$, $R_o = 2 \text{ k}\Omega$, $v_s = 5 \text{ V}$. Make sure to show the direction of current i_o .

 Δ

$$V_o = - \frac{R_F}{R_s} v_s = - \frac{5.1 \text{ k}}{1.7 \text{ k}} \times 5 \text{ V} = -15 \text{ V}$$
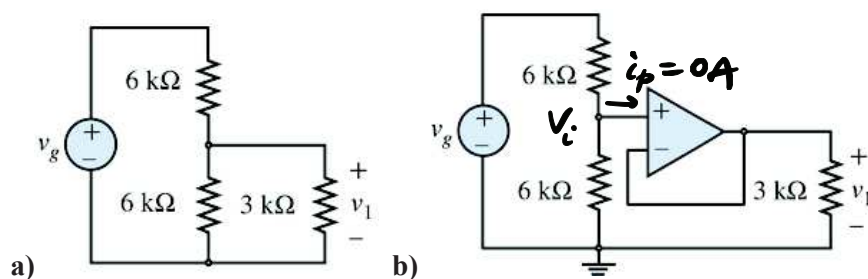
$$i_o = \frac{V_o}{R_o} = - \frac{15 \text{ V}}{2 \text{ k}} = -7.5 \text{ mA}$$



Problem 3**Figure P3**

Find v_1 in the circuits of **Figure P3 a)** and **b)**. In **Figure P3 a)** the resistor $3\text{ k}\Omega$ “loads” the output; that is, v_1 is changed by attaching the $3\text{ k}\Omega$ in parallel with the lower $6\text{ k}\Omega$ resistor. However, in **Figure P3 b)** the voltage (isolation) buffer holds v_1 to $v_g/2$, regardless of the presence of the $3\text{ k}\Omega$ resistor and its value!

△ a)

$$V_1 = \frac{(6\text{k} \parallel 3\text{k})}{6\text{k} + (6\text{k} \parallel 3\text{k})} V_g = \frac{2\text{k}}{6\text{k} + 2\text{k}} V_g = \frac{1}{4} V_g$$

voltage divider

b)

$$V_1 = V_i = \frac{6\text{k}}{6\text{k} + 6\text{k}} V_g = \frac{1}{2} V_g$$

voltage buffer $i_p = 0\text{ A}$, so we can use voltage divider



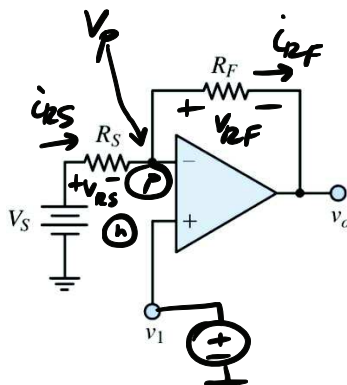
Problem 4

Figure P4

In the op-amp circuit of **Figure P4** the voltage V_1 is applied to the non-inverting terminal of the op-amp. Assuming V_S , R_S and R_F are provided, determine the resulting output voltage v_o . Will the output change if we attach to the output any non-zero resistor R_L .

△

$$V_p = V_n = V_1$$

Since $i_p = i_n = 0 \Rightarrow i_{RS} - i_{RF} = 0$

$$i_{RS} = \frac{V_{RS}}{R_S} = \frac{V_S - V_p}{R_S} = \frac{V_S - V_1}{R_S}$$

$$i_{RF} = \frac{V_{RF}}{R_F} = \frac{V_p - V_o}{R_F} = \frac{V_1 - V_o}{R_F}$$

$$\frac{V_S - V_1}{R_S} - \frac{V_1 - V_o}{R_F} = 0$$

$$\frac{V_S}{R_S} - \left(\frac{1}{R_S} + \frac{1}{R_F} \right) V_1 + \frac{V_o}{R_F} = 0$$

$$V_o = -\frac{R_F}{R_S} V_S + \frac{R_S + R_F}{R_S} V_1$$

Observe, if $V_1 = 0V$, then $V_o = -\frac{R_F}{R_S} V_S$ as expected.